
Schematic using 8:1 MUX (4 points) 74151

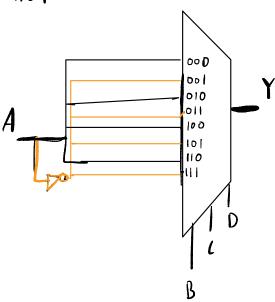

B	C	D	<b>Y</b>
0	D	0	A
0	0		Ā
0		0	A
0	1	1	Ā
1	Ö	0	A
	0	1	Ā
	1	0	A
1	l	1	71