

Schematic using only NOT, OR, AND (4 points)

$$Y = (A'D) + (A D')$$

